
VIVEKANANDA COLLEGE
THAKURPUKUR
KOLKATA-700063

NAAC ACCREDITED 'A' GRADE

**Course Title: Operational Amplifier and
Application**

**Topic: Basic Operational Amplifier , Opamp
application**

Paper: CC8 theory

Unit: Fourth Semester

Semester:

Name of the Teacher: Debarati Sarkar

Name of the Department: Electronics

Operational Amplifiers



An operational amplifier is a dc coupled high-gain electronic voltage amplifier with a differential i/o and usually, a single ended output. In this configuration, an op-amp produces an output potential that is typically hundreds of thousands of times larger than the potential difference between its i/o terminals.

Why is it called operational amplifier?
Op-amp stands for operational amplifier because they were used to model the basic mathematical operations of addition, subtraction, integration, differentiation etc in electronic analog computers.


Characteristics of Operational Amplifier

- Infinite open loop gain $G_v = V_{out}/V_{in}$
- Infinite i/p impedance R_{in}
- Zero i/p offset voltage range.
- Infinite o/p voltage range.
- Infinite bandwidth with zero phase shift and infinite slew rate.
- Zero output impedance R_{out}
- Zero noise
- Infinite common-mode rejection ratio (CMRR)

Op-AMP Block diagram

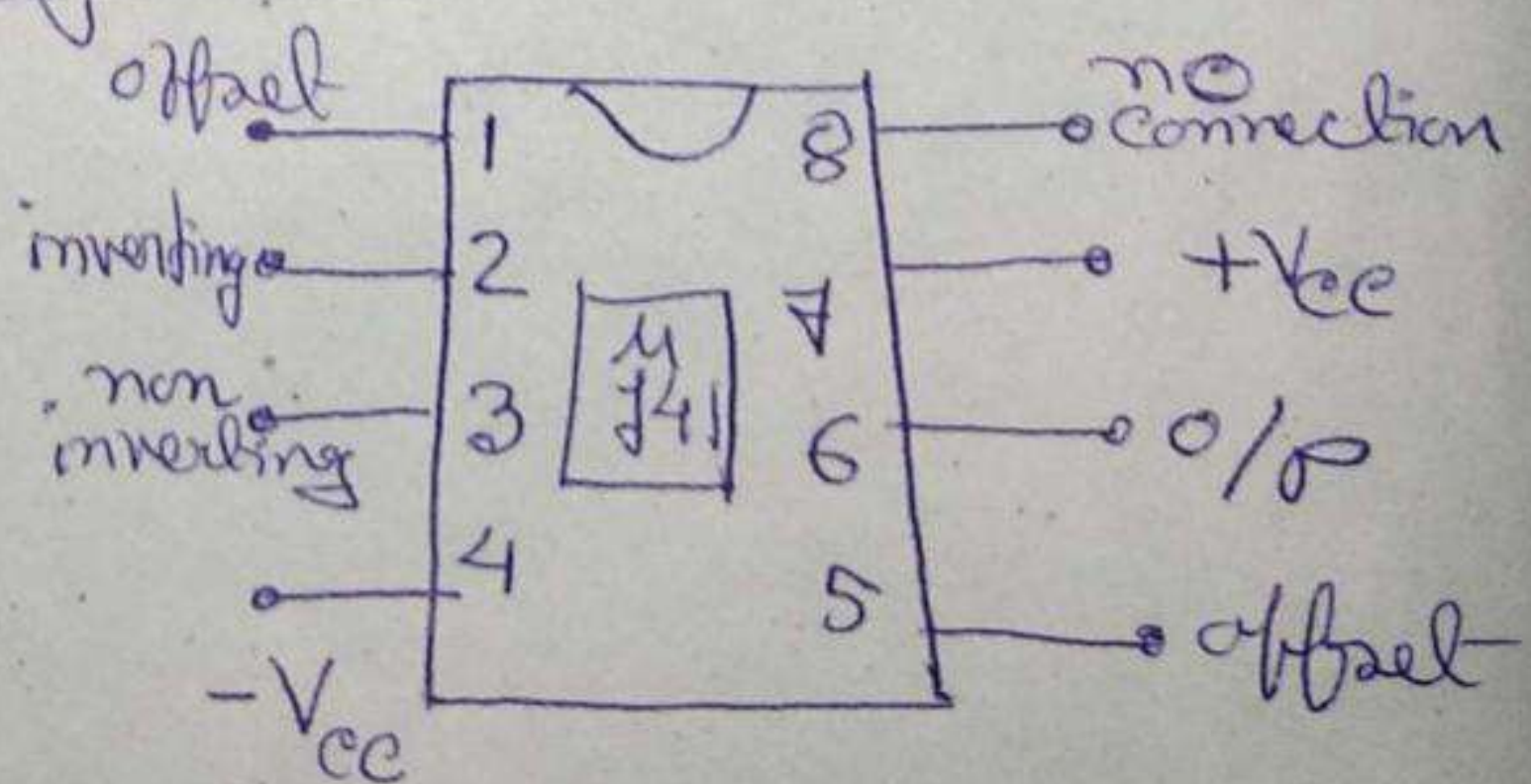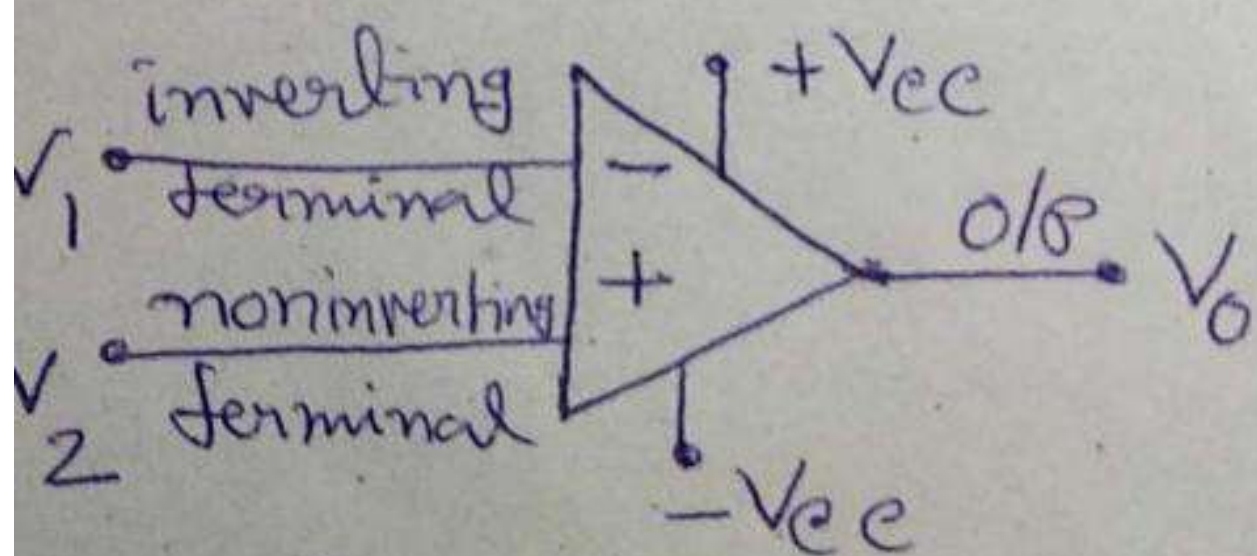

OP- Amp Application :-

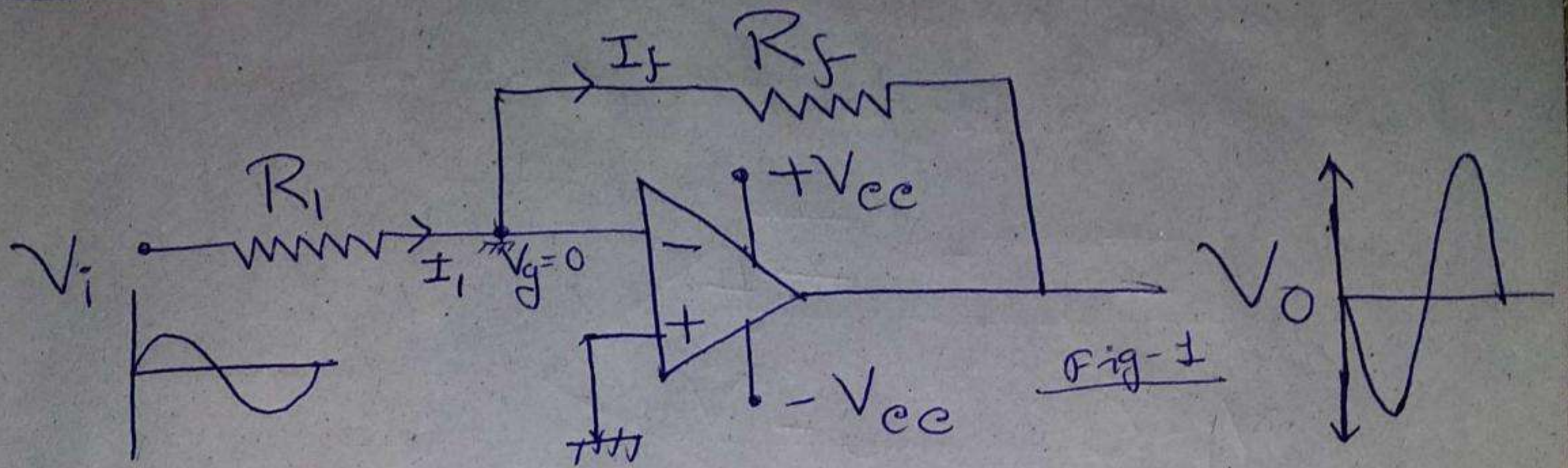

In this Inverting Amplifier circuit the operational amplifier is connected with feedback to produce a closed loop operation.

Here the i/o voltage V_i is connected to the negative terminal of the op-amp and the positive terminal is grounded. R_i is called the i/o resistance b/w the input voltage and inverting terminal of the op-amp and the feedback resistance R_f is connected b/w the inverting terminal and o/o terminal of the op-amp. In this amplifier, the amplifier o/o is inverted and amplified. Here the o/o is 180° phase shift.

Virtual ground :- In Op-Amps the term virtual ground means that the voltage at that particular node is almost equal to ground voltage (0V). It is not physically connected to ground. A virtual ground is a result of an op-amp trying to keep its two i/o terminals at the same potential when used in a feedback circuit. Real ground is when a terminal is connected physically to the ground or earthed to complete the circuit with phase.

According to the KCL

the entering currents in the circuit = the leaving currents ^{from} the circuit


$$\therefore I_i = I_f$$

$$a) \frac{V_i - 0}{R_i} = \frac{0 - V_o}{R_f}$$


$$b) \frac{V_i}{R_i} = -\frac{V_o}{R_f}$$

$$c) \boxed{V_o = -\frac{R_f}{R_i} V_i}$$
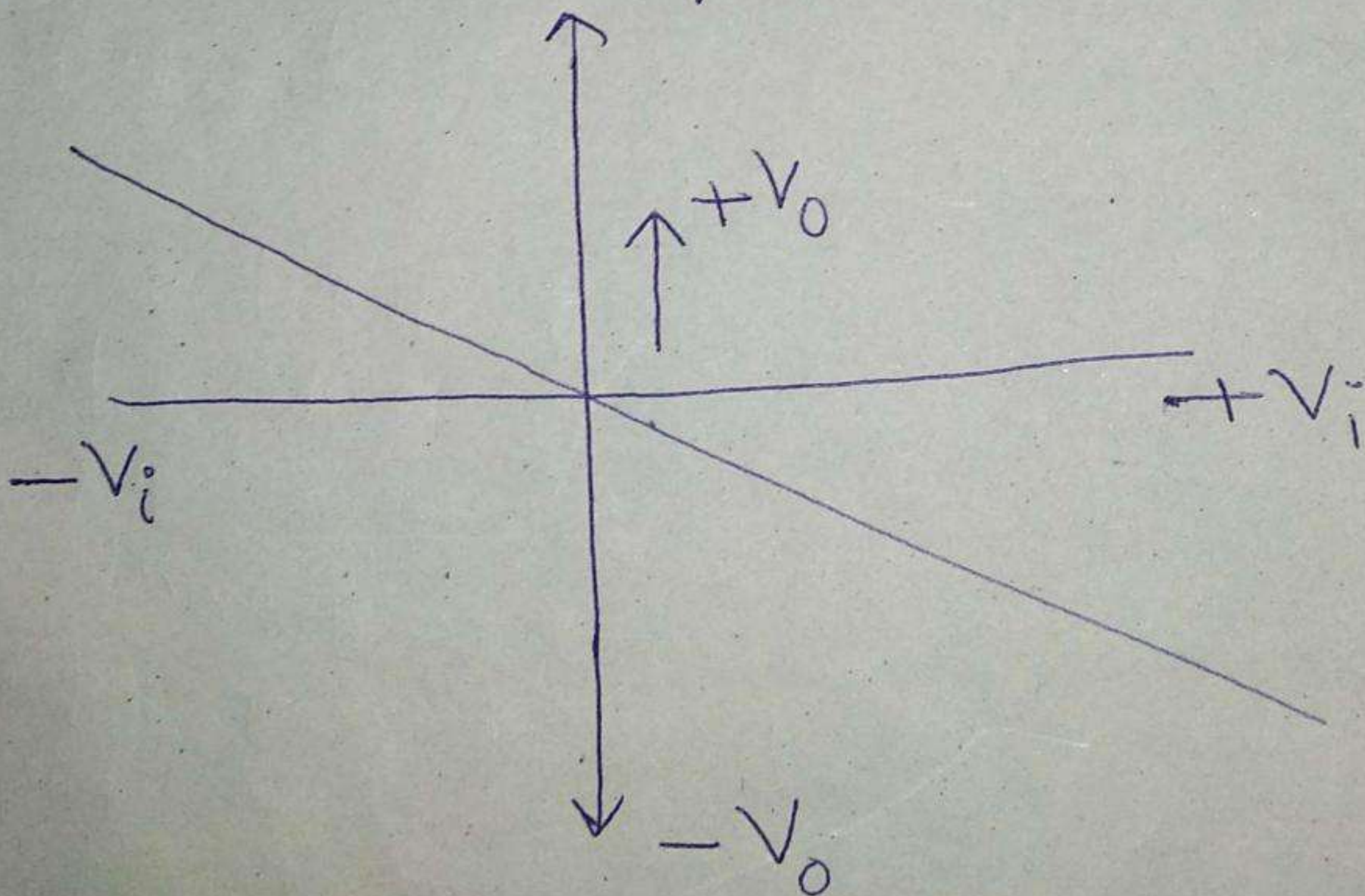
$$\text{Gain} = A = \frac{V_o}{V_i} = -\frac{R_f}{R_i}$$



Non-Inverting Amplifier

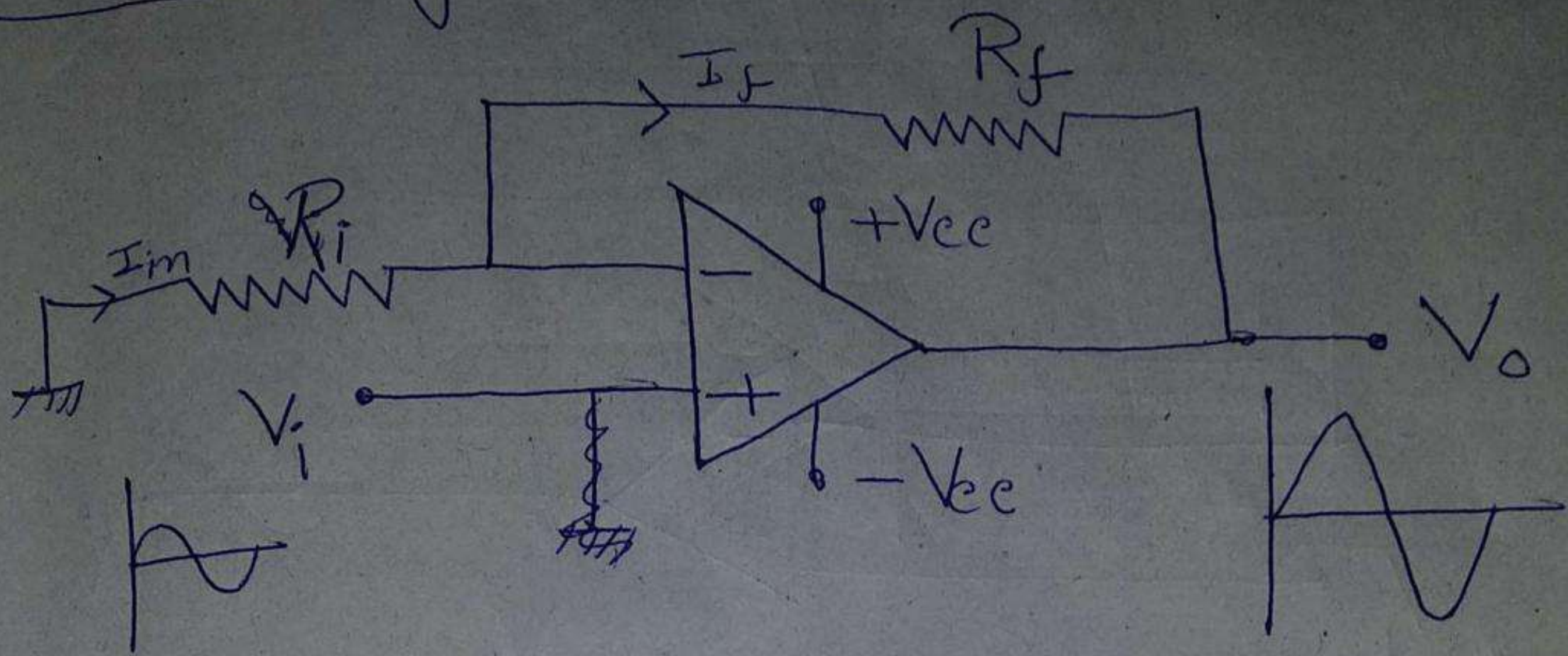


Here $V_i = \frac{V_o R_f}{R_i + R_f}$

$$V_o = \left(\frac{R_i + R_f}{R_i} \right) V_i$$


$$V_o = \left(1 + \frac{R_f}{R_i} \right) V_i$$

$$\text{gain} = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}$$

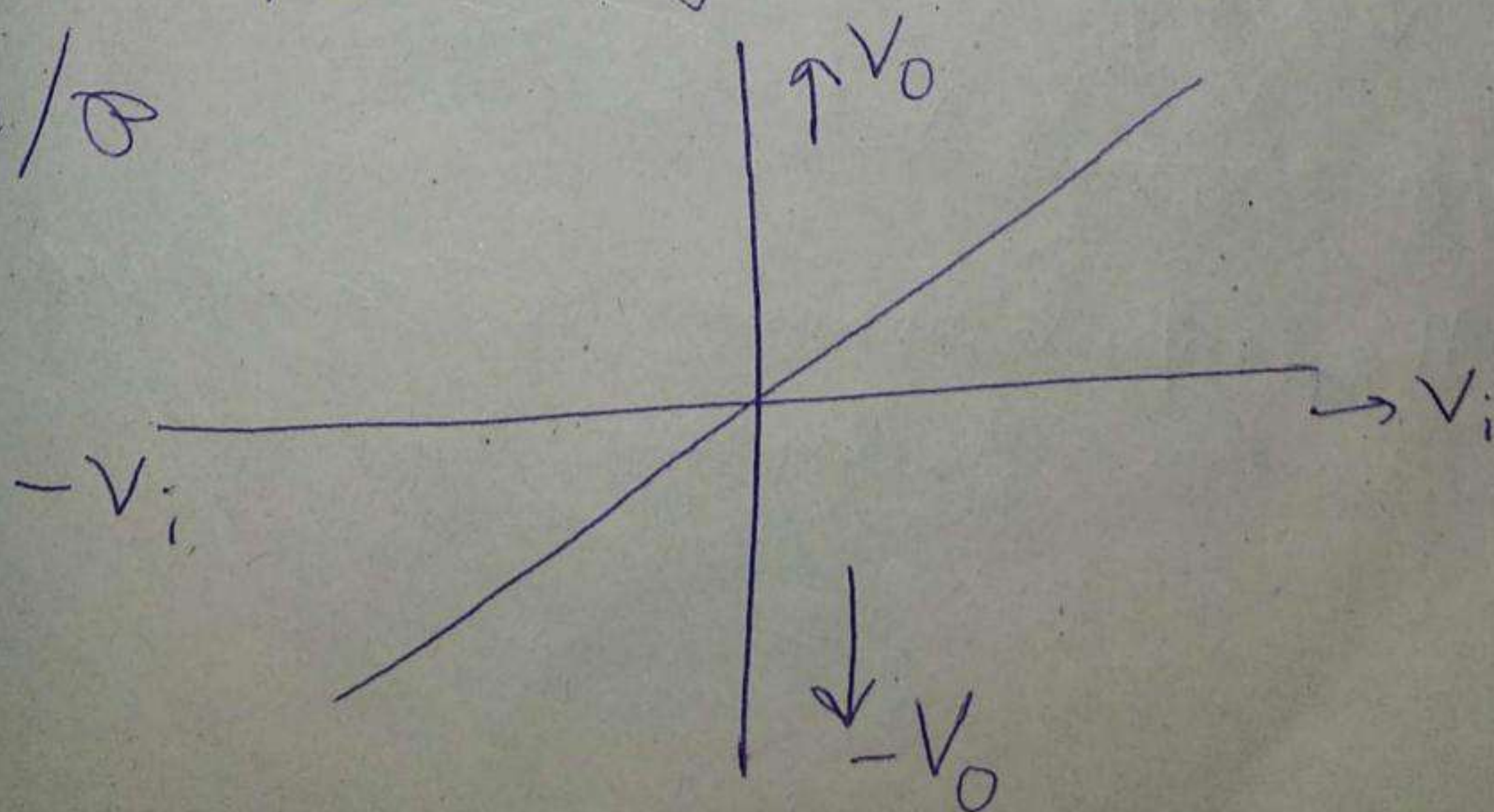Here the o/p voltage is in phase to the i/p



Unity gain buffer / Voltage follower

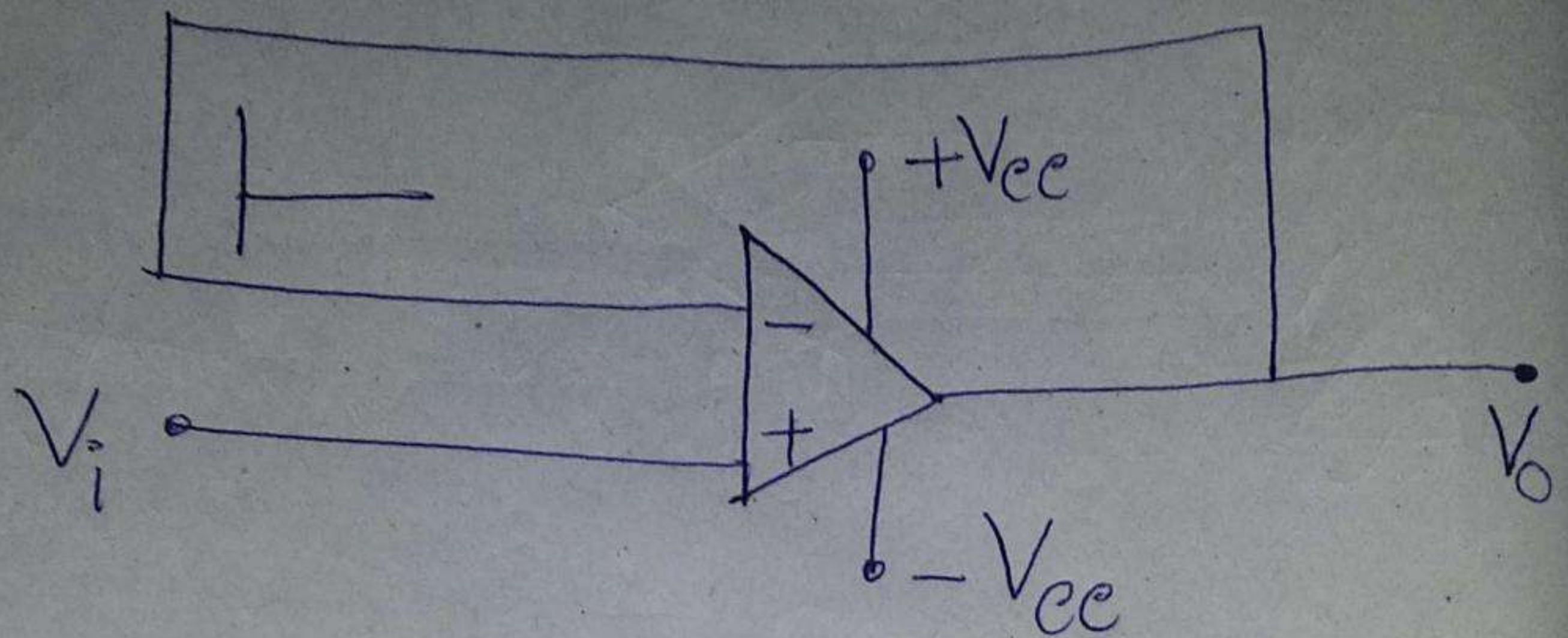

^A
Q. unity gain buffer / Voltage buffer:
~~Here~~ is a op-amp circuit which has a voltage gain of 1. This means that the op-amp does not provide any amplification to the signal. The reason it is called a unity gain buffer (or amplifier) is because it provides a gain of 1, meaning there is no gain, the o/p voltage signal is the same as the i/o signal voltage.

Here the input resistance is open and the feedback resistance closed.


$$R_i = \infty, R_f = 0$$

$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_i$$

$$V_o = \left(1 + \frac{0}{\infty}\right) V_i$$

$$V_o = V_i$$

Summing Amplifier :-

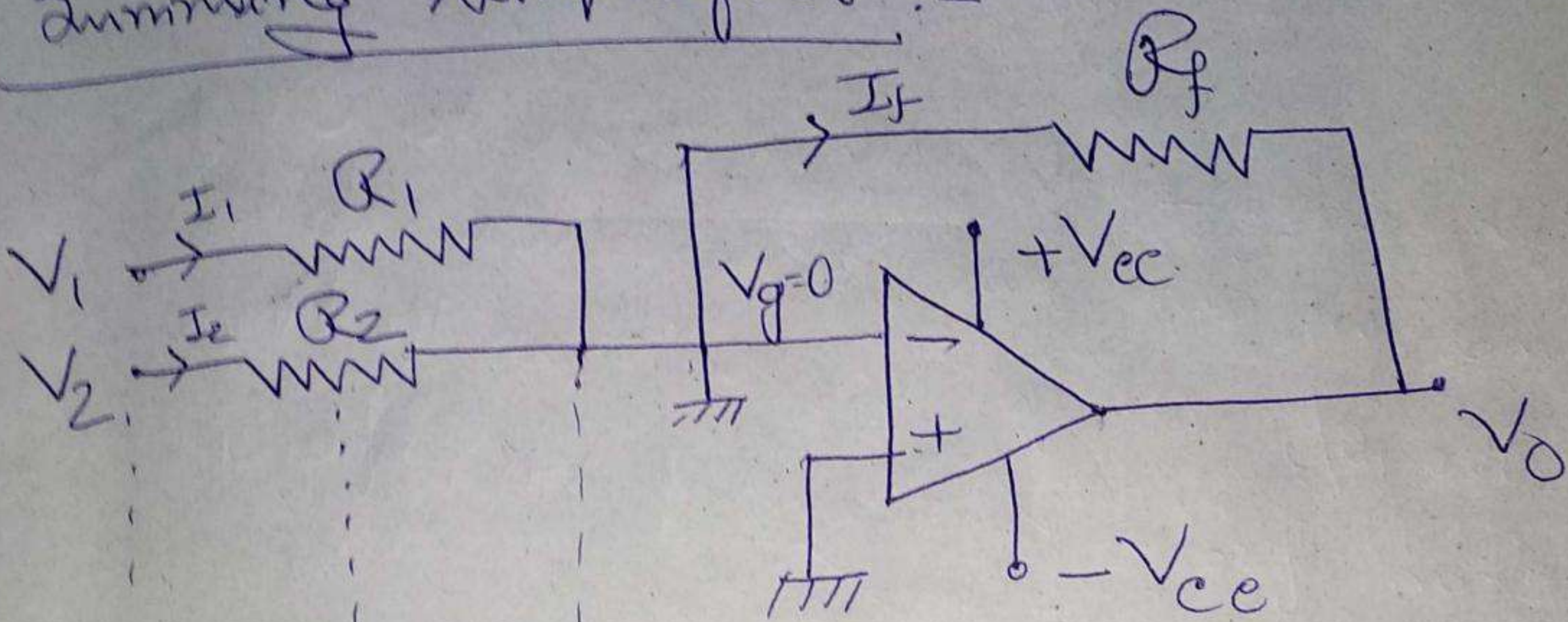

According to KCL

$$I_1 + I_2 + \dots + I_n = I_f$$

$$\therefore \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} = \frac{0 - V_o}{R_f}$$

$$\therefore \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} = -\frac{V_o}{R_f}$$


$$\therefore V_o = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right)$$

∴ $R_1 = R_2 = \dots = R_n = R$

$$\therefore V_o = -\frac{R_f}{R} (V_1 + V_2 + \dots + V_n)$$

if $R_f = R$ $V_o = -(V_1 + V_2 + \dots + V_n)$

Differential Amplifier / Subtractor

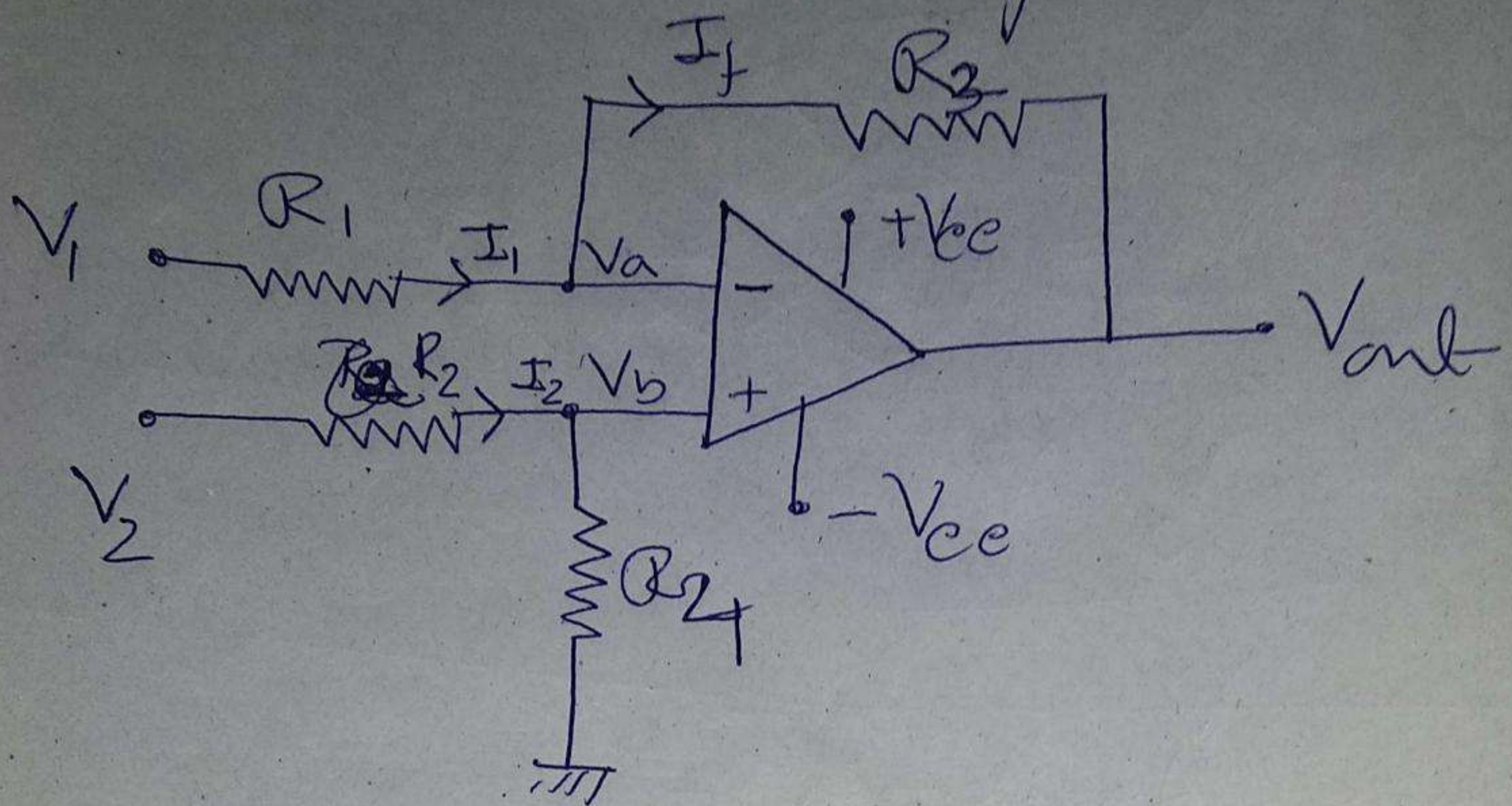

By connecting each i/p in turn to 0V ground we can use superposition to solve for the o/p voltage V_{out} . Then the transfer function for a differential Amplifier ckt is given as:

$$I_1 = \frac{V_1 - V_a}{R_1}, \quad I_2 = \frac{V_2 - V_b}{R_2},$$

$$I_f = \frac{V_a - V_{out}}{R_3}$$

Summing Point $V_a = V_b$

$$V_b = \frac{V_2 R_2}{R_4 + R_2}$$

if $V_2 = 0$ then $V_{out}(a) = -V_1 \left(\frac{R_3}{R_1} \right)$

if $V_1 = 0$ $V_{out}(b) = V_2 \left(\frac{R_4}{R_2 + R_4} \right) \left(\frac{R_1 + R_3}{R_1} \right)$

$$V_{out} = -V_{out}(a) + V_{out}(b)$$

$$= -V_1 \left(\frac{R_3}{R_1} \right) + V_2 \left(\frac{R_4}{R_2 + R_4} \right) \left(\frac{R_1 + R_3}{R_1} \right)$$

When resistors, $R_1 = R_2$ and $R_3 = R_4$ the above transfer function for the differential amplifier can be simplified to the following expression

$$V_{out} = V_2 \left(\frac{R_3}{R_1 + R_3} \right) \left(\frac{R_1 + R_3}{R_1} \right) - V_1 \left(\frac{R_3}{R_1} \right)$$


$$V_{out} = V_2 \left(\frac{R_3}{R_1} \right) - V_1 \left(\frac{R_3}{R_1} \right)$$

$$V_{out} = \frac{R_3}{R_1} (V_2 - V_1)$$

If all the resistors are all of the same ohmic value, that is $R_1 = R_2 = R_3 = R_f$ then the circuit will become a Unity Gain Differential Amplifier and the voltage gain of the amplifier will be exactly one or unity. Then the o/p expression would simply be

$$V_{out} = V_2 - V_1$$

Op-AMP as Integrator

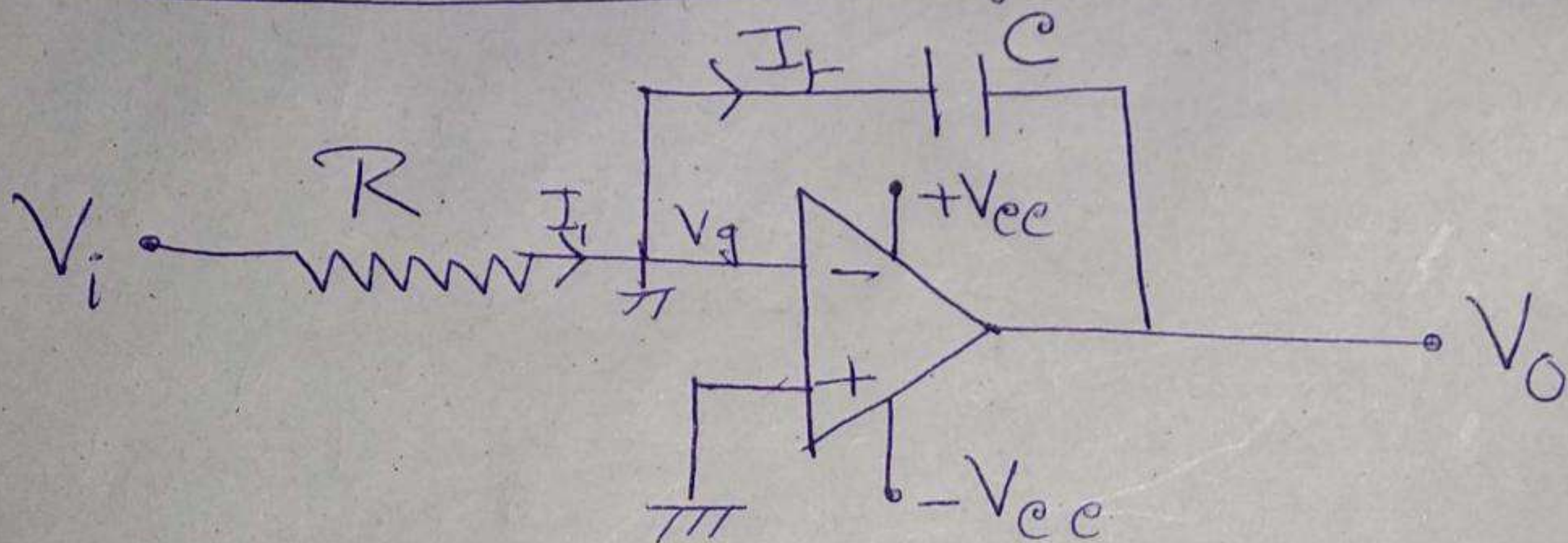

The input current $I_i = \frac{V_i}{R}$

The feedback current $I_f = \frac{dq}{dt}$

$$\therefore I_f = -\frac{d(cV_o)}{dt}$$

$$\therefore I_f = C \frac{dV_o}{dt}$$

$$I_i = I_f$$

$$\frac{V_i}{R} = -C \frac{dV_o}{dt}$$

$$\frac{V_i}{RC} = - \frac{dV_o}{dt}$$

$$\frac{dV_o}{dt} = - \frac{V_i}{RC}$$


$$\frac{dV_o}{dt} = - \frac{1}{RC} V_i$$

$$dV_o = - \frac{1}{RC} V_i dt$$

$$\int dV_o = - \frac{1}{RC} \int_0^t V_i dt$$

$$V_o = - \frac{1}{RC} \int_0^t V_i dt$$

Op differentiator

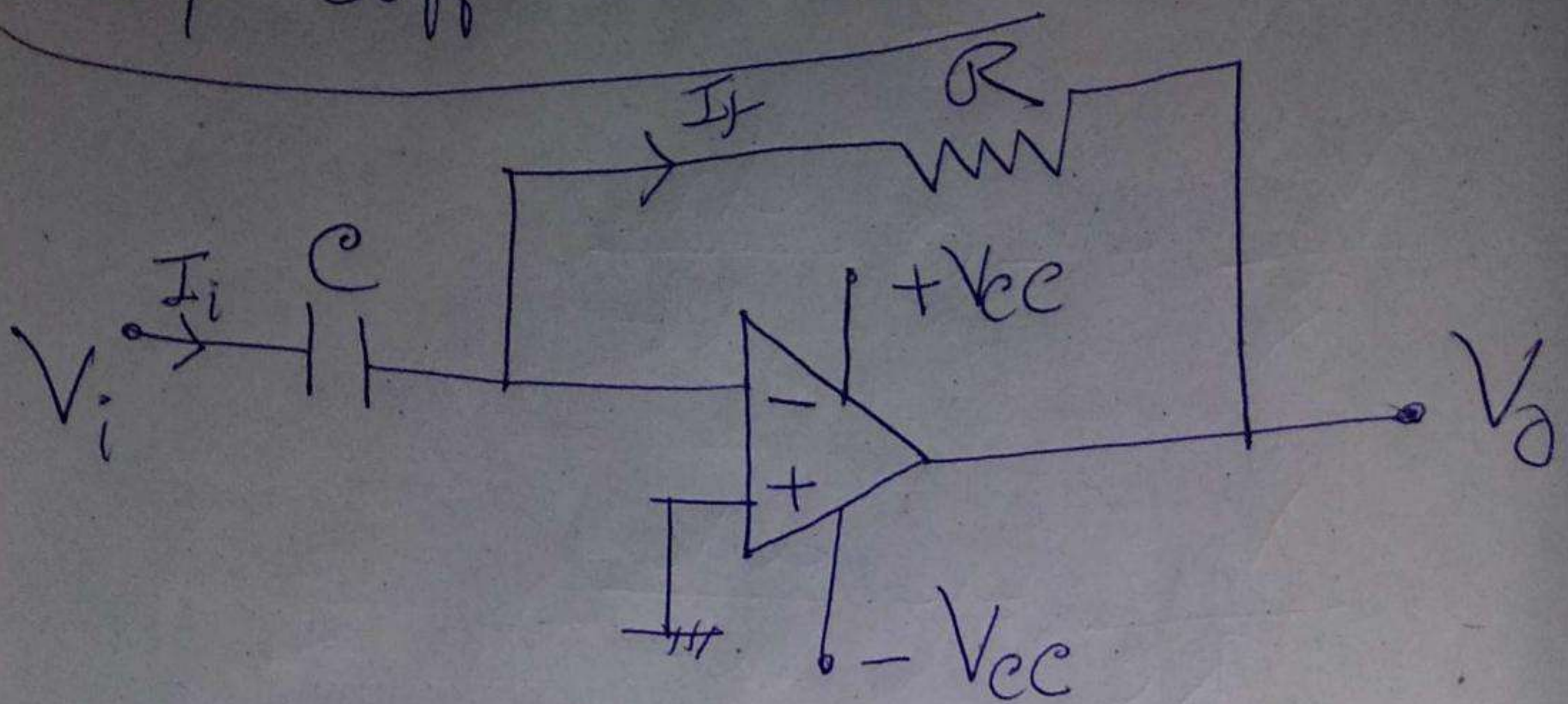

$$I_i = \frac{dq}{dt}$$
$$= \frac{d(c v_i)}{dt}$$

$$= c \frac{d v_i}{dt}$$

$$I_f = + \frac{0 - v_o}{R} = - \frac{v_o}{R}$$

According to KCL

$$I_i = I_f$$


$$c \frac{d v_i}{dt} = - \frac{v_o}{R}$$

or

$$v_o = - R c \frac{d v_i}{dt}$$

Current to Voltage Converter :-

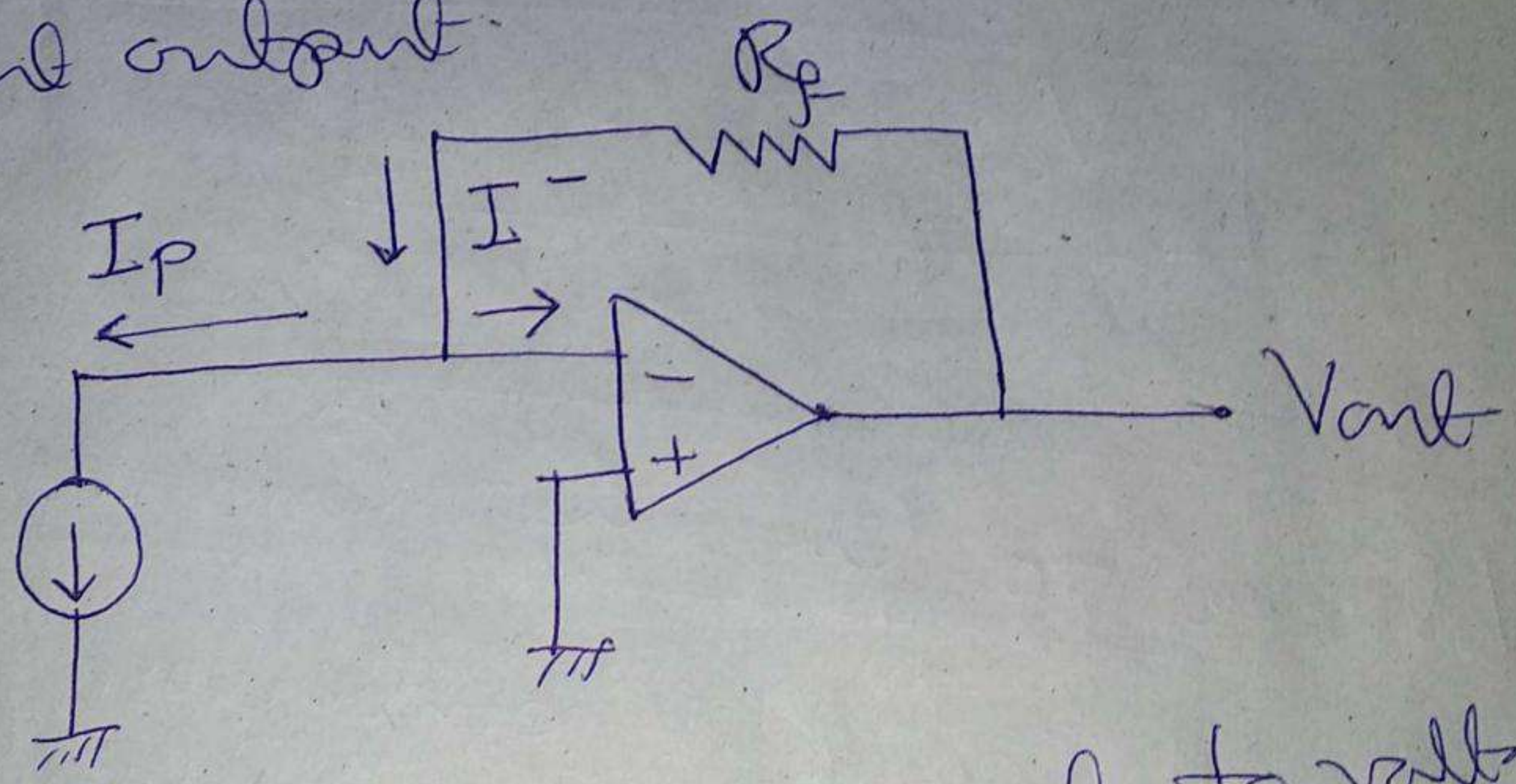A current to voltage converter will produce a voltage proportional to the given ~~current~~ current. This circuit is ~~required~~ required if your ~~measuring~~ measuring instrument is capable only of measuring voltages and you need to measure the current output.



To analysis the current to voltage converter by inspection.

- If we apply KCL to the node at V^- (the inverting i/o) and let the i/o current to the inverting i/o be I_- , then

$$\frac{V_{out} - V^-}{R_f} = I_p + I_-$$

- Since the output is connected to V_- through R_f , the op-amp is in a negative feedback.


$$V_- = V_+ = 0$$

and assume assuming that I^- is 0 and simplifying.

$$V_{out} = I_o R_f$$

Voltage to Current Converter:-

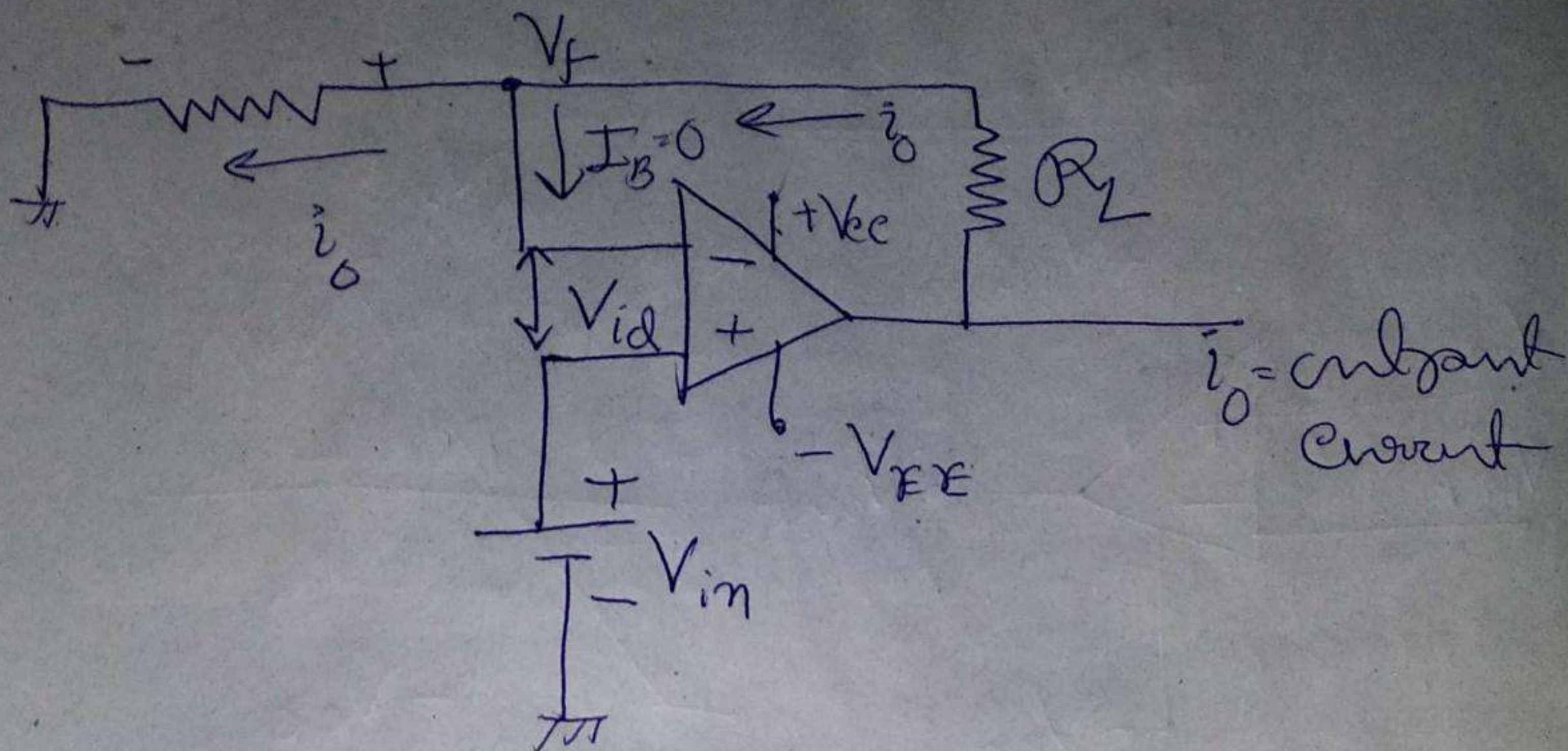Voltage to current converter in which load resistor R_L is floating (not connected to ground). V_{in} is applied to non-inverting input terminal, and the feedback voltage across R_f across the inverting input terminal.



Writing KVL for the i/o loop.


Voltage $V_{id} = V_f$ and $I_B = 0$,

$$V_i = R_L i_o$$

where $i_o = V_i / R_L$

From the fig input voltage V_{in} is converted into output current of V_{in} / R_L . In other words, input volt appears across R_L . If R_L is a precision resistor, the output current ($i_o = V_{in} / R_L$) will be precisely fixed.

Comparators

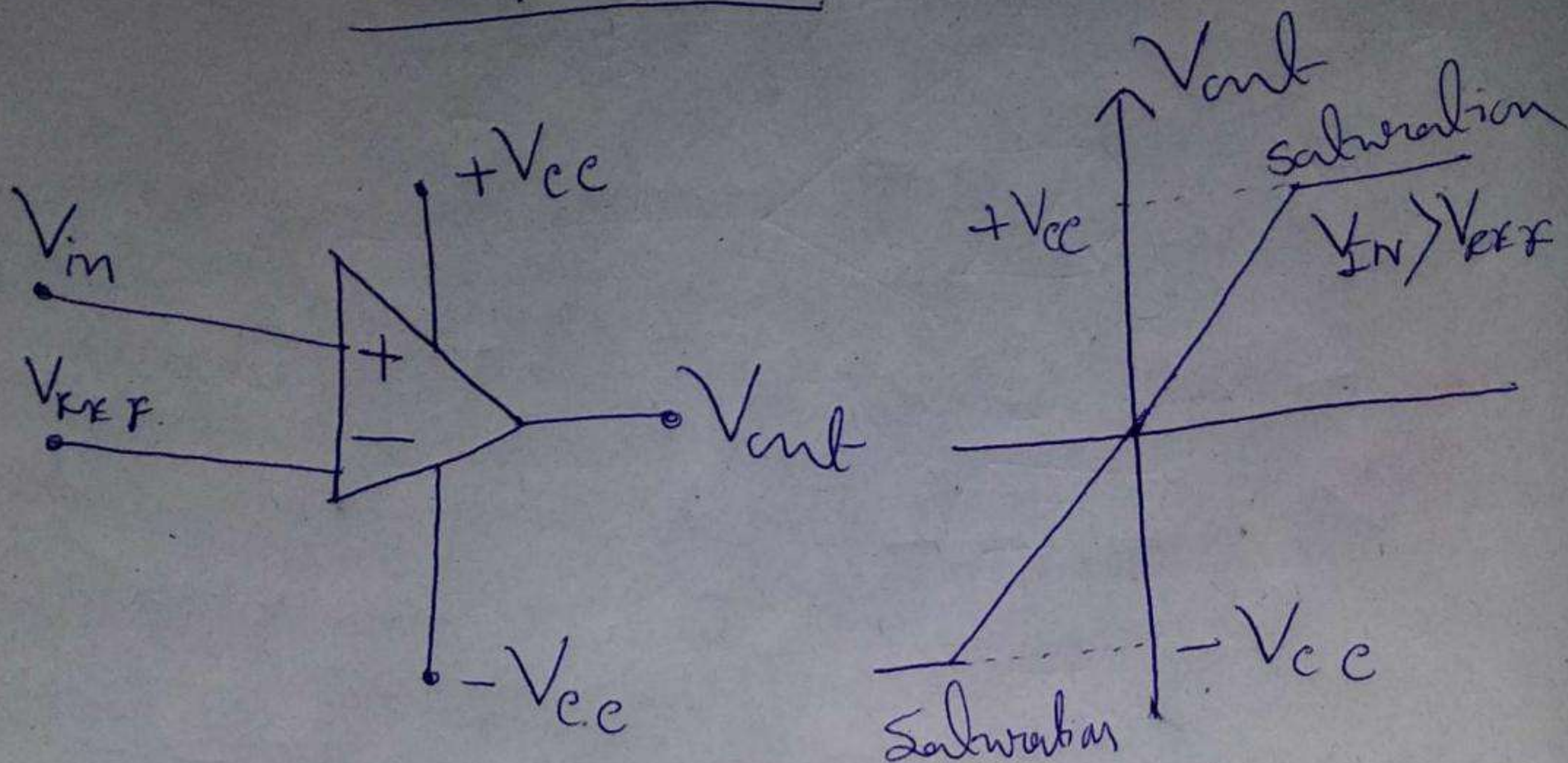

The Op-AMP comparator compares one analogue voltage level with another analogue voltage level or some present reference voltage, V_{REF} and produces an output signal based on this voltage comparison. In other words, the op-amp voltage comparator compares the magnitudes of two voltage i/p's and determines which is the largest of the two.


With reference to the op-amp comparator circuit above, let's first assume that V_{in} is less than the DC voltage level at V_{REF} , ($V_{in} < V_{REF}$). As the non-inverting (+ve) i/p of the comparator is less than the inverting (negative) i/p, the o/p will be LOW and at the negative supply voltage, $-V_{CC}$ resulting in a negative saturation of the o/p.

If we now increase the i/p voltage, V_{IN} so that its value is greater than the reference voltage V_{REF} on the inverting i/p, the o/p voltage rapidly switch HIGH towards the +ve supply voltage, $+V_{CC}$ resulting in a positive saturation of the o/p. If we reduce again the i/p voltage V_{IN} so that it is slightly less than the reference voltage, the op-amp's o/p switches back to its negative saturation voltage acting as a threshold ~~data~~ detector.

Schmitt Trigger

When operating an Op-Amp in the open loop mode where a feedback is not used, for example, in a Basic Comparator Circuit, the very large open loop gain of the Op-AMP will cause the smallest of noise voltage to trigger the comparator.

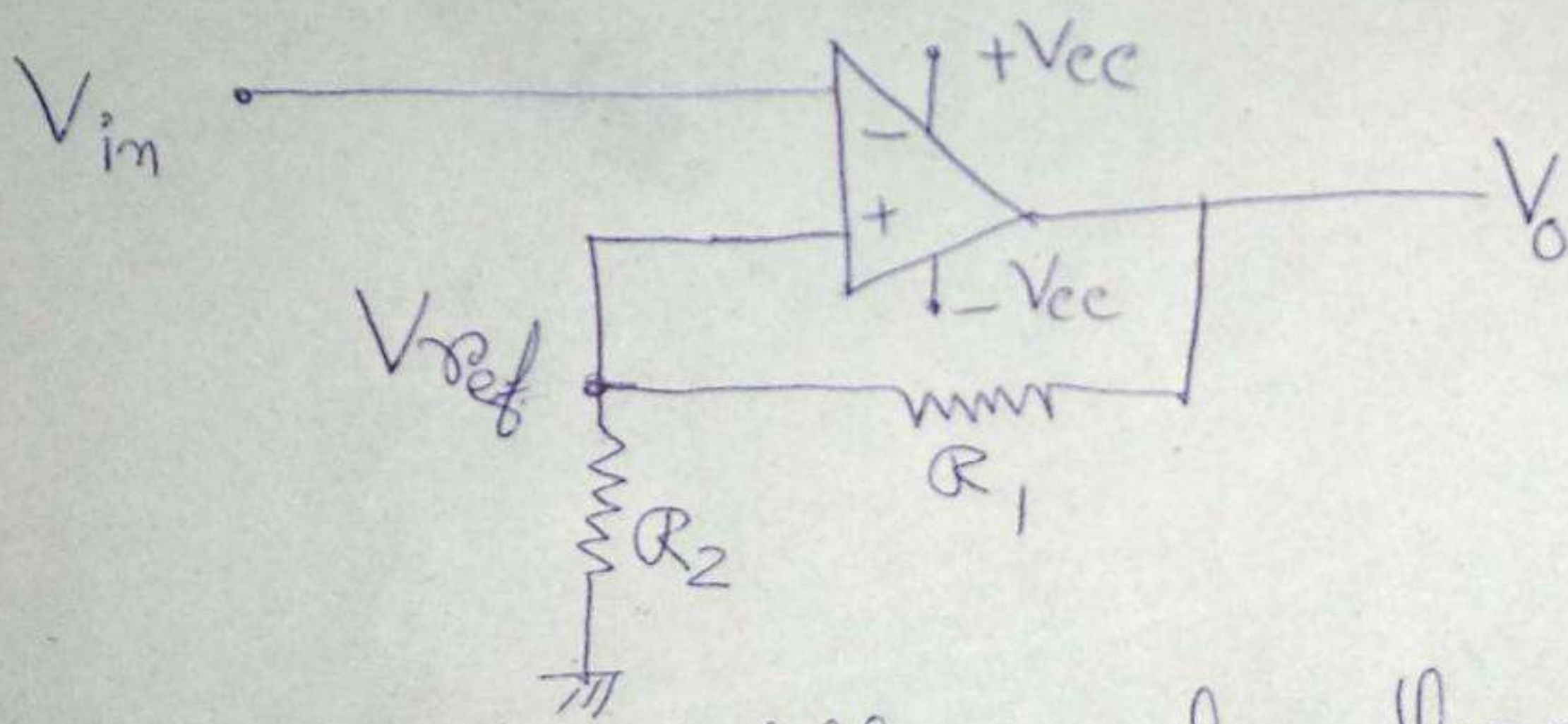In an Inverting Schmitt Trigger, the i/o is applied to the inverting terminal of the Op-AMP. In this mode, the o/p produces is of opposite polarity.



When V_{in} is slightly greater than V_{ref} , the o/p becomes $-V_{sat}$ and it becomes $-V_{ref}$, the V_{in} is slightly less than $-V_{ref}$, the o/p becomes V_{sat} . Hence the o/p voltage V_o is either at V_{sat} or $-V_{sat}$ and the i/o voltage at which these state changes occur can be controlled using R_1 and R_2 .

The values of V_{ref} and $-V_{ref}$ can be formulated as:

$$V_{ref} = \frac{V_0 R_2}{R_1 + R_2} \quad V_{ref} = \frac{V_0 R_2}{R_1 + R_2}$$

$$V_0 = V_{sat}$$

Hence $V_{ref} = \frac{V_{sat} \times R_2}{R_1 + R_2}$

$$-V_{ref} = \frac{V_0 R_2}{R_1 + R_2}$$

$$V_0 = -V_{sat}$$

$$\therefore -V_{ref} = -\frac{V_{sat} R_2}{R_1 + R_2}$$

The reference voltage V_{ref} and $-V_{ref}$ are called Upper Threshold Voltage V_{UT} and Lower Threshold Voltage V_{LT} .

The following image shows the output voltage versus i/p voltage graph, also known as the Transfer Characteristic of Schmitt Trigger.

