

VIVEKANANDA COLLEGE THAKURPUKUR KOLKATA-700063

NAAC ACCREDITED 'A' GRADE



Topic: Flip-flop conversion

Course Title: Digital Electronics and VHDL

Paper: ELT-A-CC-4-09-TH

Unit: Sequential Circuit

Semester: Fourth

Name of the Teacher: Arpita Das

Name of the Department: Electronic Science

Realisation of one flip-flop using other flip-flop

① To realise a flip-flop (X) using another flip-flop (Y) →

steps

(i) obtain present state - next state (PS-NS) table for flip-flop (X)

ii) use the excitation or application table of flip-flop (Y), add the values to the present-state-next state table.

iii) using K-maps, simplify the logic expressions for excitation inputs of flip-flop (Y) and design next-state decoder logic.

* next-state decoder — flip-flop (Y) along with a combinational circuit is called NEXT state decoder.

① Realisation of D-Flip-flop using S-R Flip-flop.

i) D is the (X) flip-flop

ii) S-R is (Y) - flip flop

iii) PS-NS table of D-Flip flop

Q_n	D	Q_{n+1}
0	0	0
0	1	1
1	0	0
1	1	1

iv) application table of SR flip-flop

Q_n	Q_{n+1}	Excitation inputs	
		S	R
0	0	0	d
0	1	1	0
1	0	0	1
1	1	d	0

v) Excitation table for D flip-flop using S-R

Q_n	D	Q_{n+1}	Excitation inputs	
			S	R
0	0	0	0	d
0	1	1	1	0
1	0	0	0	1
1	1	1	d	0

(iv) For K-MAP from excitation maps.

Excitation map for S

$Q_n \backslash D$	0	1
0	0	1
1	0	d


$S = D$

Excitation map for R

$Q_n \backslash D$	0	1
0	d	0
1	1	0

$R = \bar{D}$

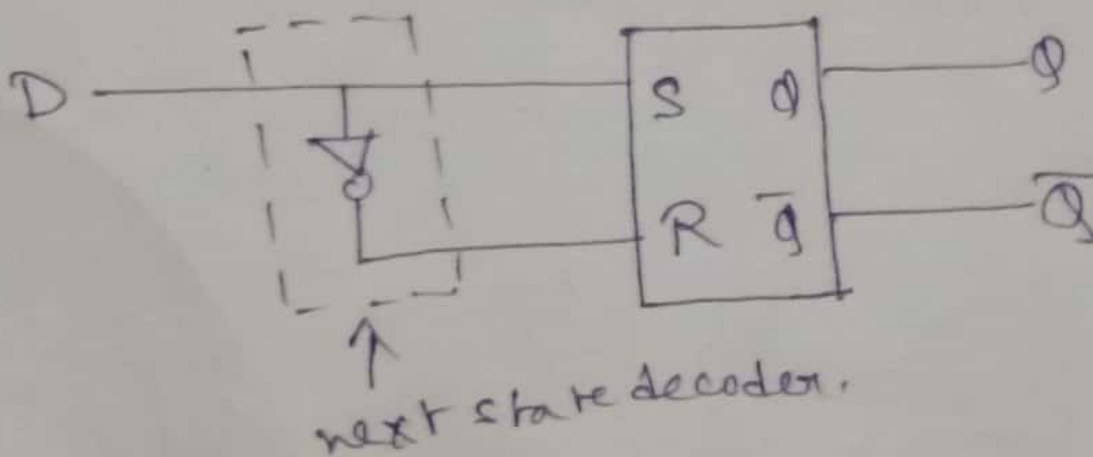or from above K-MAP. construct D flip-flop using S-R flip-flop



Realisation of J-K flip-flop using S-R flip-flop.

i) PS-NS table for J-K flip-flop.

Q_n	J	K	Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

ii) using application table of S-R flip-flop realise Excitation table for J-K flip-flop.

Q_n	J	K	Q_{n+1}	Excitation inputs	
				S	R
0	0	0	0	0	d
0	0	1	0	0	d
0	1	0	1	1	0
0	1	1	1	1	0
1	0	0	1	d	0
1	0	1	0	0	1
1	1	0	1	d	0
1	1	1	0	0	1

(v) Excitation map for S


Q_n / JK	00	01	11	10
0	0	0	1	1
1	d	0	0	d

$$S = J\bar{Q}_n$$

(vi) Excitation table for R

Q_n / JK	00	01	11	10
0	d	d	0	0
1	0	1	1	0

$$R = KQ_n$$

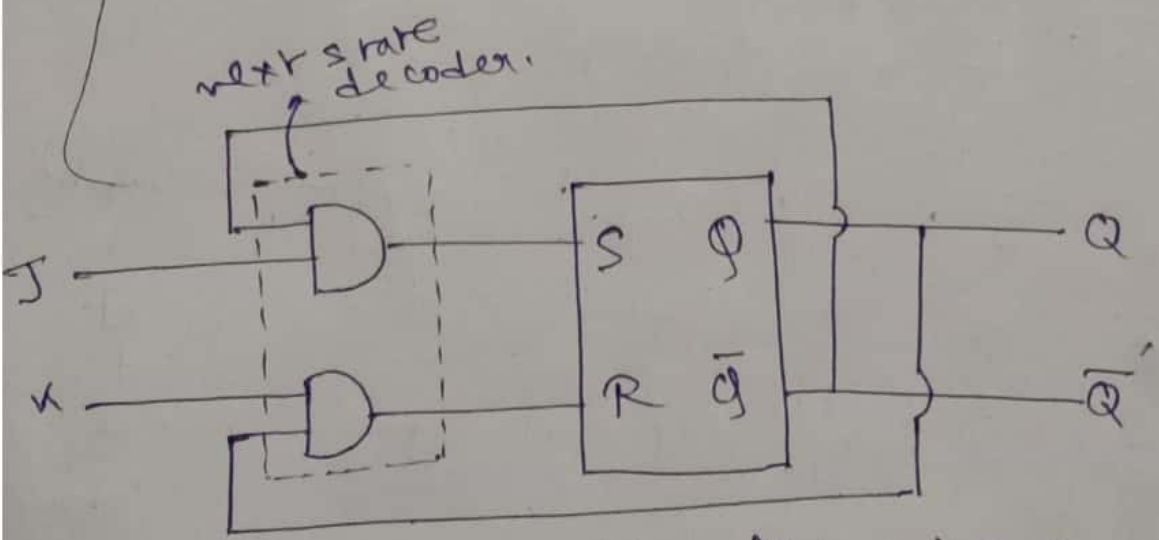

J-K flip flop using S-R.

Realisation of T Flip-flop using D Flip flop :-

i) PS-NC table of T Flip-flop.

Q_n	T	Q_{n+1}
0	0	0
1	0	1
0	1	1
1	1	0


ii) Next the table shows characteristic table of T flip flop along with the excitation input of D Flip-flop

T	Q_t	Q_{t+1}	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

iii) K-map for D

Q_n \ T	0	1
0	0	1
1	1	0

$$D = T \oplus Q_n$$

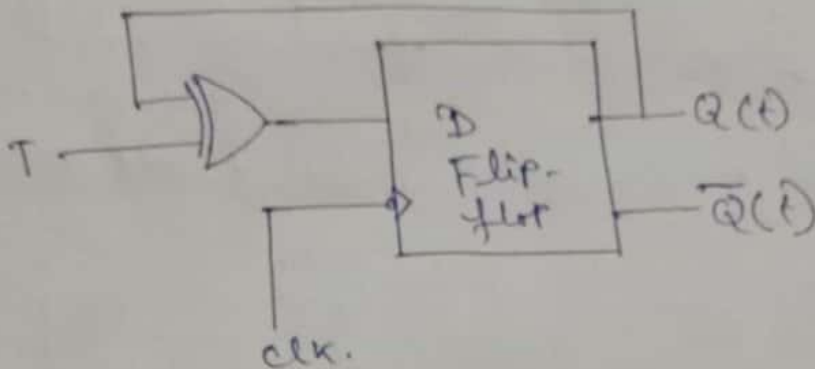

T flip flop using D flip flop

Realisation of D Flip-flop using JK Flip-flop :-


i) PS-NS table of D flip-flop

Q_n	D	Q_{n+1}
0	0	0
0	1	1
1	0	0
1	1	1

ii) Excitation table for D flip-flop realization using J-K flip-flop


Q_n	D	Q_{n+1}	Excitation inputs	
			J	K
0	0	0	0	d
0	1	1	1	d
1	0	0	d	1
1	1	1	d	0

iii) K-map for J

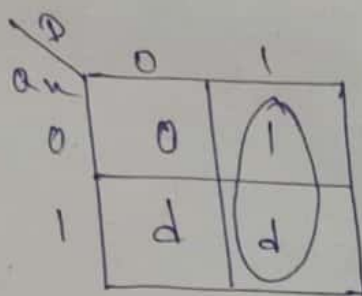


$$J = D$$

K-map for K

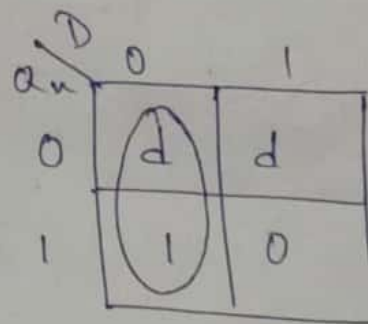

$$K = \bar{D}$$

iv)

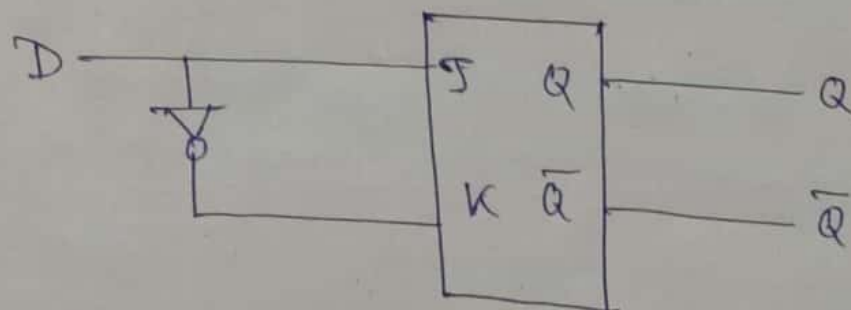

D flip flop using k-flip-flop

Realisation of T-flip-flop using J-K Flip-flop :-

i) PS-NS table of T Flip-flop

T	Q_n	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

ii) Excitation table for T flip-flop realisation using J-K Flip-flop.

T	Q_n	Q_{n+1}	Excitation inputs	
			J	K
0	0	0	0	d
0	1	1	d	0
1	0	1	1	d
1	1	0	d	1

iii) K-map for J


	Q_n	0	1
T	0	0	d
	1	1	d

$$J = T$$

K-Map for K

	Q_n	0	1
T	0	d	0
	1	d	1

$$K = T$$

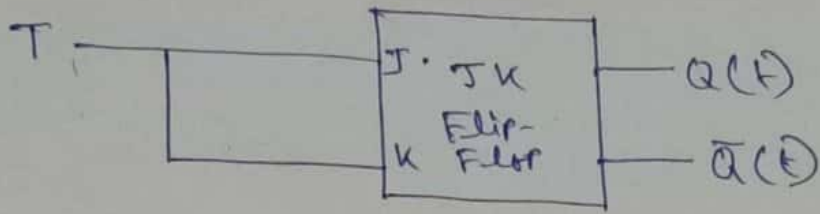

T flip flop using J-k Flip-flop.