

VIVEKANANDA COLLEGE  
THAKURPUKUR  
KOLKATA-700063

NAAC ACCREDITED 'A' GRADE



Topic: thyristor

Course Title: Electronics device and circuit

Paper: CMS-A-CC-2-4-TH

Unit: power device

Semester: second


Name of the Teacher: Arpita Das

Name of the Department: Electronic Science
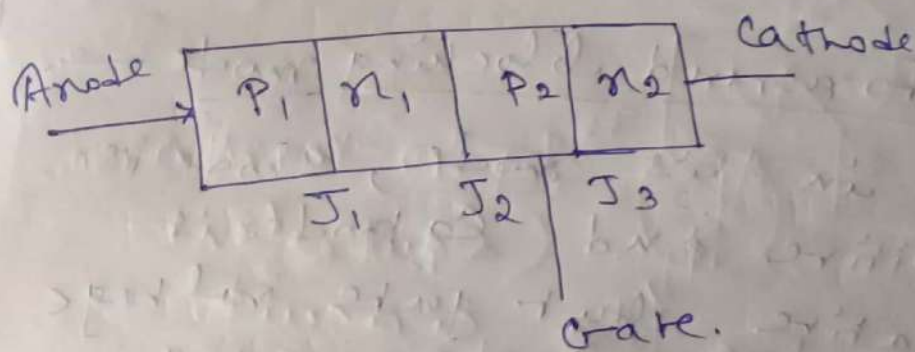
# Semiconductor Controlled Rectifier

SCR (semiconductor controlled Rectifier or silicon controlled Rectifier) is a four-layer state current-controlling device. SCR also called thyristor.


It is a four-layer P-N-P-N device having three P-N junction,  $J_1$ ,  $J_2$ ,  $J_3$  in series.



The  $n_1$  layer is much wider than other regions and it has lower doping level for high break-down voltage. The contact electrode to outer p-layer is called anode and outer n-layer is called cathode. The gate electrode is connected to inner p-layer.

The three terminal device is commonly called SCR.

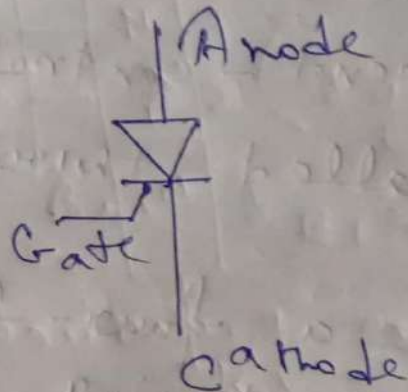An SCR is diagrammatically represented by  $\rightarrow$



### Modes of operation in SCR

#### ① Forward blocking mode —

in this mode, anode is positive and Cathode is negative but gate voltage is zero or disconnected.

So Junctions  $J_1, J_3 \rightarrow$

forward bias and  $J_2$  reverse bias.

If reverse bias voltage of  $J_2$  increases after avalanche value, it starts to conduct.

Below this value, SCR is off state.

## ii) Forward conducting mode —

An SCR is brought to on state by increasing potential difference between anode and cathode — or by applying a positive signal at gate. After on state, gate voltage is no longer needed to maintain.

SCR can be switched off by →

i) Decreasing anode current below the lowest value called holding current.

ii) By reverse the voltage of anode and cathode.



## iii) Reverse blocking mode —

In this mode, Cathode is made positive w.r. to anode,

Then  $J_1, J_3$  — reverse biased and  $J_2$  is forward biased.

In this mode, a small leakage current flows through it

→ Two transistor Analogy  
of SCR :-

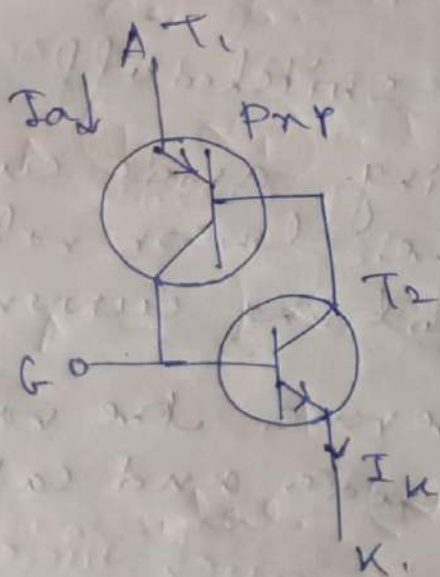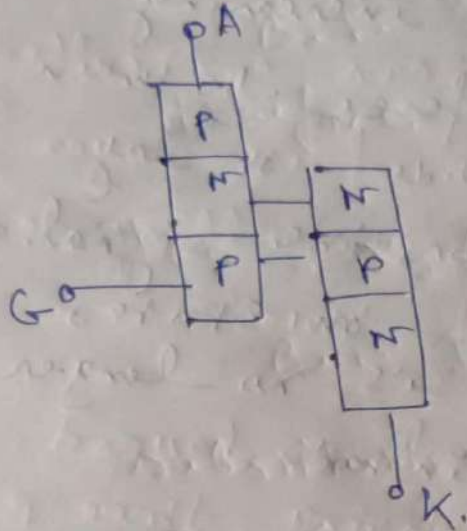

Two transistor equivalent circuit.

The collector of each transistor is connected to the base of the other.

Assume, load resistance is connected between anode and cathode and small voltage is applied at gate. when there is no gate voltage the  $T_2$  is in cut-off

and no current flows through collector, and hence Base of  $T_1$ .

When a particular voltage is applied between gate and Cathode, a small base current flows through the base of  $T_2$  and  $I_c$  increase. And hence  $I_B$  at  $T_1$  drives the transistor into saturation and  $I$  will flow from anode to Cathode.

$I_{B2} = I_{c1}$  and  $I_{c2} = I_{B1}$   
Current through cathode

$$I_K = I_G + I_A \quad \text{--- (1)}$$

$$I_{B1} = I_{E1} - I_{c1} \quad \text{--- (2)}$$

and  $I_{c1} = \alpha_1 I_{E1} + I_{c01}$  --- (3)

$I_{c0}$  - leakage current.

Substitute eq. 3 in eq. 2.

$$I_{B1} = I_{E1} (1 - \alpha_1) - I_{c01} \quad \text{--- (4)}$$

The emitter  $I$  of  $T_1$

$$I_A = I_{E1}$$

$$I_{B1} = I_A (1 - \alpha_1) - I_{c01}$$

For  $T_2$

$$I_{C2} = \alpha_2 I_{E2} + I_{C02}$$

$$\text{But } I_U = I_{E2}$$

$$\text{Therefore } I_{C2} = \alpha_2 I_U + I_{C02}$$

$$I_{C2} = \alpha_2 (I_g + I_A) + I_{C02} \quad \text{--- (5)}$$

$$\text{But } |I_{B1}| = I_{C2} \quad \text{--- (6)}$$

substituting eq 4 and 5 in

eq. 6.

$$I_A (1 - \alpha_1) - I_{C01} = \alpha_2 (I_g + I_A) + I_{C02}$$

$$I_A = \frac{[\alpha_2 I_g + I_{C01} + I_{C02}]}{1 - (\alpha_1 + \alpha_2)}$$

① when  $(\alpha_1 + \alpha_2) < 1$

② when  $(\alpha_1 + \alpha_2) = 1$  then device goes to non-conducting state to conducting state.